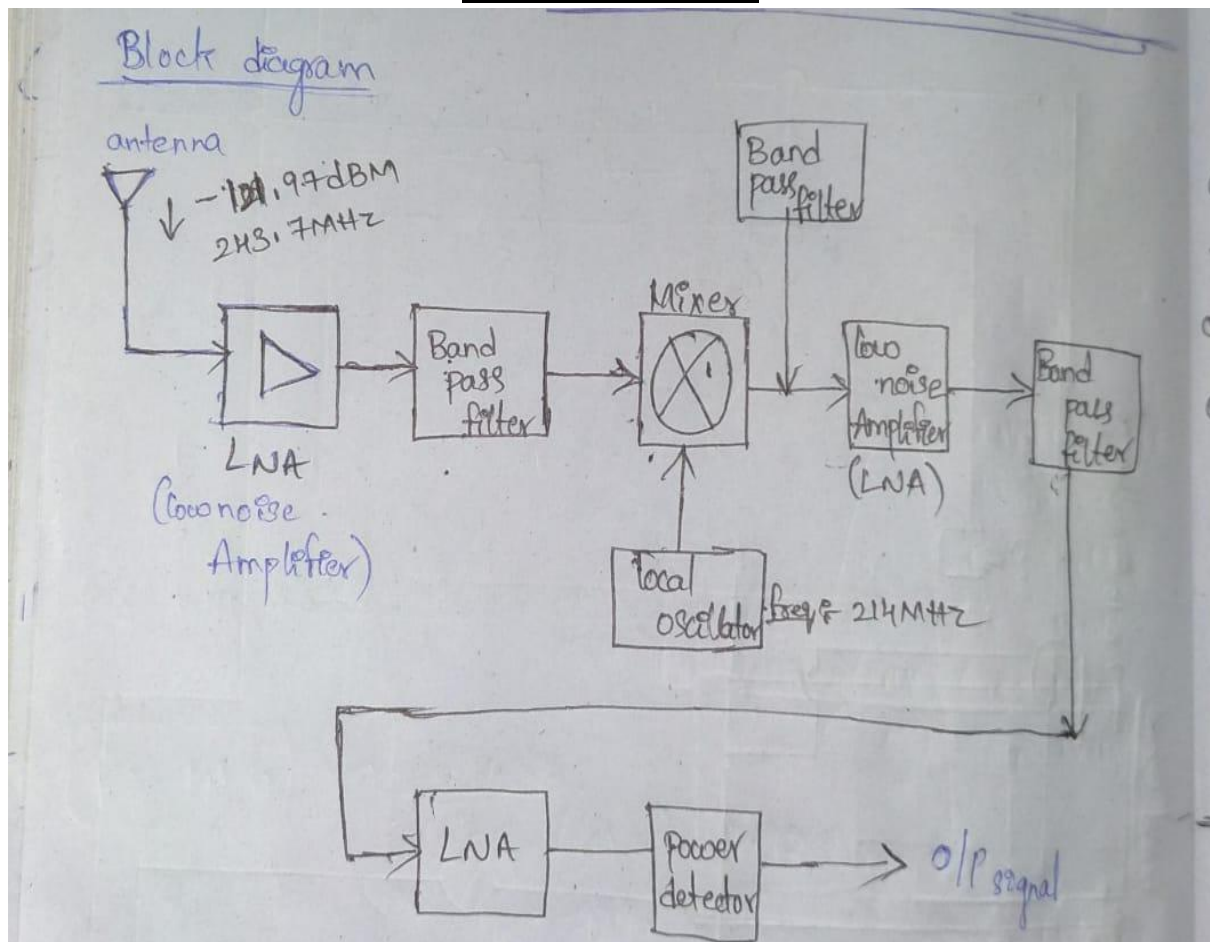


Theoretical Explanation of the project and calculations



Note : filters = these are passive Elements which don't generate noise, but it generates Attenuation of signal which affects the gain (decrement).

LNA, mixers = Exhibits noise changes and have impact on overall receiver noise factor. (Have Low NF LNA can detect weak signals) (So, we have to select the accurate LNA and mixers which have low NF and ~~low~~
 1) Mixer have low Gain loss , 2) LNA have high Gain)

Theoretical calculation using Friis formula

$$F_{\text{total}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots + \frac{F_n - 1}{G_1 G_2 \dots G_n}$$

Power in from satellite to antenna of receiver is,

$$P_{\text{in}} = -129.97 \text{ dBm}$$

And frequency coming from the satellite to the receiver antenna is,

$$f_{\text{in}} = 243.7 \text{ MHz}$$

where using Friis formula calculating each and every component noise figure and power out and overall receiver cascaded noise and power out and frequency out from the receiver (Demodulate the frequency as our requirement by using local oscillator)

F_1, F_2, F_3 = Noise factors of the individual stages (not in dB)

G_1, G_2, \dots = Gains of preceding stages (not in dB)

$$\text{Noise factor (F)} = (10^{\text{NF (dB)}})/10$$

$$\text{Gain (G)} = (10^{\text{Gain (dB)}})/10$$

Start from first component the calculation of noise factor (where overall noise can be determined through overall noise factor (F))

$$\underline{\text{LNA}} \Rightarrow \text{NF} = 1.5, \text{Gain} = 25$$

$$F_1 = 10^{\text{NF}}/10 = 10^{1.5}/10 = 1.412$$

$$G_1 = 10^{25}/10 = 3162$$

$$\underline{\text{BPF}} \Rightarrow \text{NF} = 1.5, \text{Gain} = 25 \Rightarrow F_2 = 1.412$$

(for filters there is no change in gain) G_2 = No Gain factor

$$\underline{\text{Mixer}} \Rightarrow \text{NF} = 1.5, \text{Gain} = 3$$

In Mixer we have (-3 dB loss), so Gain reduced

$$G_3 = 10^{15/10} = 1.412, \quad G_3 = 10^{23/10} = 5.011$$

BPF \Rightarrow NF = 1.5, Gain = 0 (for filters there is no change in Gain)
 $f_4 = 1.412, \quad G_4 = 10^{22/10} = \text{No gain factor}$

LNA \Rightarrow NF = 1.5, Gain = 20
 $f_5 = 1.412, \quad G_5 = 10^{20/10} = 100$

BPF \Rightarrow NF = 1.5, Gain = 0 (No change of)
 $f_6 = 1.412, \quad G_6 = \text{No gain factor, Gain \& NF}$

LNA \Rightarrow NF = 1.5, Gain = 30
 $f_7 = 1.412, \quad G_7 = 10^{30/10} = 1 \times 10^3$

Power detector \Rightarrow No change of any parameter

$$S_o, f = f_1 + \frac{f_2 - 1}{G_1} + \frac{f_3 - 1}{G_1 G_2} + \dots$$

$$f = 1.412 + \frac{1.412 - 1}{3.162} + \frac{1.412 - 1}{(3.162)(5.011)} + \frac{1.412 - 1}{(3.162)(5.011)(1 \times 10^2)}$$

$f = 1.56 \Rightarrow$ convert to dB.
 $= 10 \log_{10}(1.56) = 1.93 \text{ dB}$

Power calculation $\Rightarrow P_{in} = -121.97 \text{ dBm} \Rightarrow -121.97$

LNA \Rightarrow Gain = 20 = $P_{out} = +20$

BPF \Rightarrow Attenuation = 2 = $P_{out} = -2$

modulator \Rightarrow Gain = -3 = $P_{out} = -3$

BPF \Rightarrow Attenuation = 0 = $P_{out} = 0$

LNA \Rightarrow Gain = 20 = $P_{out} = +20$

BPF \Rightarrow Attenuation = 2 = $P_{out} = -2$

LNA \Rightarrow Gain = 30 = $P_{out} = +30$

power detector \Rightarrow Gain = 0 = $P_{out} = 0$

Final $P_{out} = -53.97$

Gain

$$\text{LNA} = 25 = +25$$

$$\text{BPF} = 0 = 0$$

$$\text{Mixer} = -3 = 22$$

$$\text{BPF} = 0 = 22$$

$$\text{LNA} = 20 = 42$$

$$\text{BPF} = -2 = 40$$

$$\text{LNA} = 30 = 70$$

$$\boxed{\text{Gain}_{\text{out}} = 70 \text{ dB}}$$

frequency

$$f_{\text{in}} = 243.7 \text{ MHz}$$

$$\text{LNA} = \text{No change} = 243.7 \text{ MHz}$$

$$\text{BPF} = \text{No change} = 243.7 \text{ MHz}$$

Mixer = due to local oscillator which has 214 MHz can reduce the 214 MHz from 243.7 MHz frequency of the signal as per our requirement for accurate output signal.

$$= 243.7 - 214 = 29.75 \text{ MHz}$$

Further LNA, BPF, power detector

No change

$$\text{So, } \boxed{f_{\text{out}} = 29.75 \text{ MHz}}$$

